



① Cap across Battery Hook up on Board

② 1.5MΩ = 2 sec Lights
3.3MΩ = 5 sec Lights

③ 12 v 5Ah Lead-Acid Battery

④ Power MOSFET P10NK60ZFP
But any simple MOSFET will work

⑤ All wires For Horns are 18AWG Not 22.